

what's the address map of the memory modules?

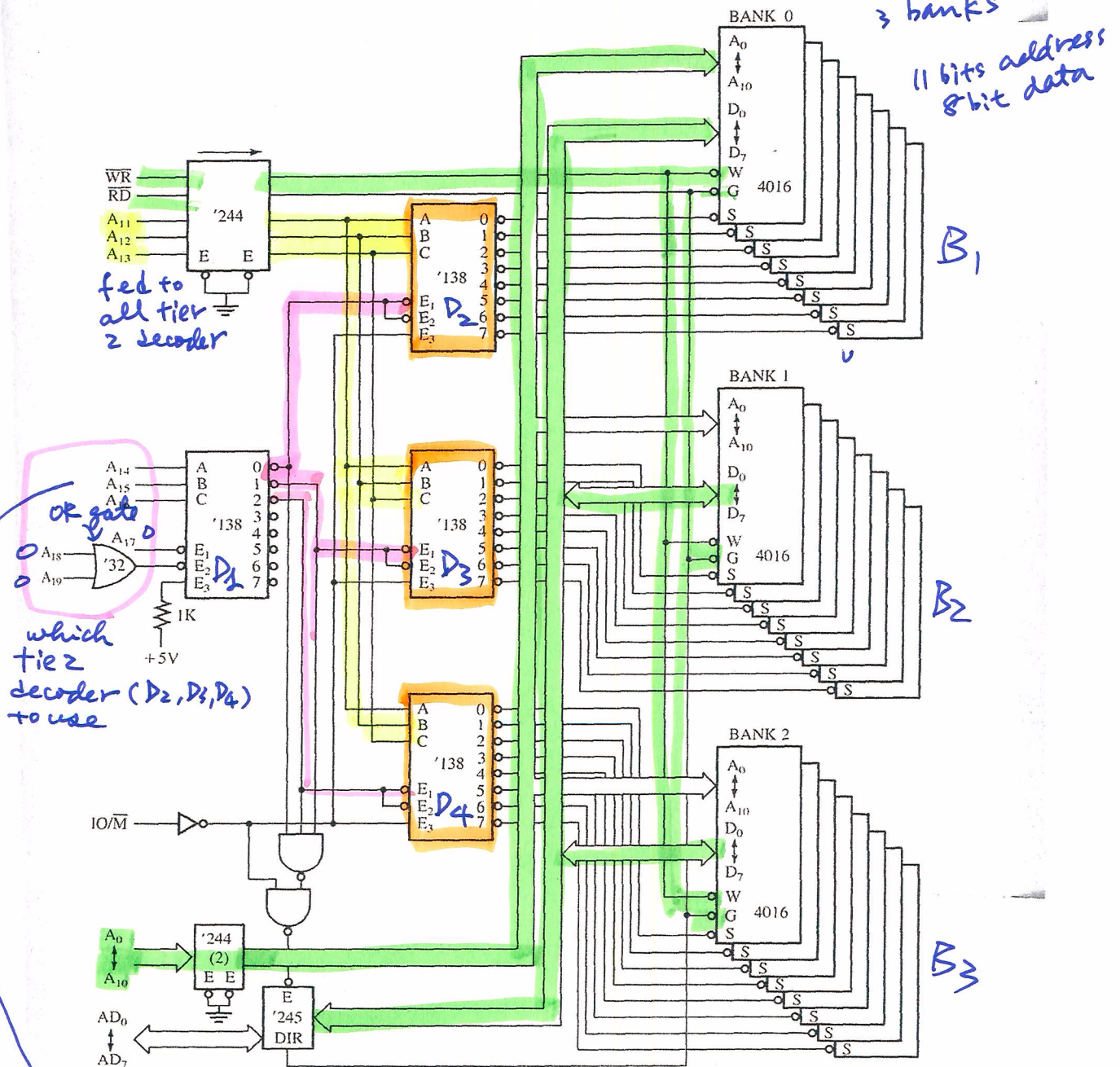


FIGURE 7-18 A 48K x 8 memory system using twenty-four TMS4016 SRAMs.

19 18 17 16 15 14 A₁₃ A₁₂ A₁₁ A₁₀ — A₀
 0 0 0 0 0 0 (B₁)
 0 0 1 (B₂)
 0 1 0 (B₃)

subject to the output of decoder 1